
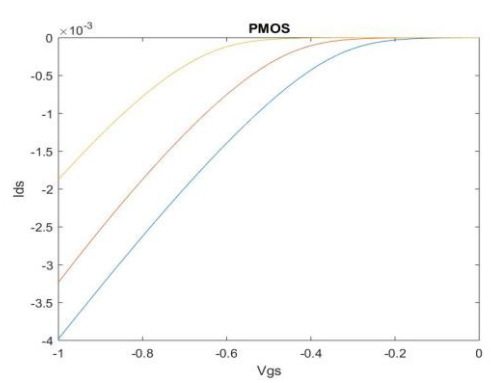
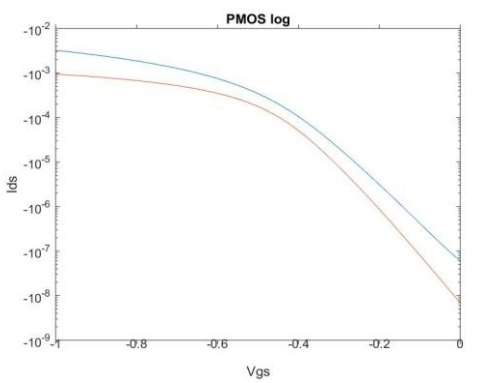
 
 
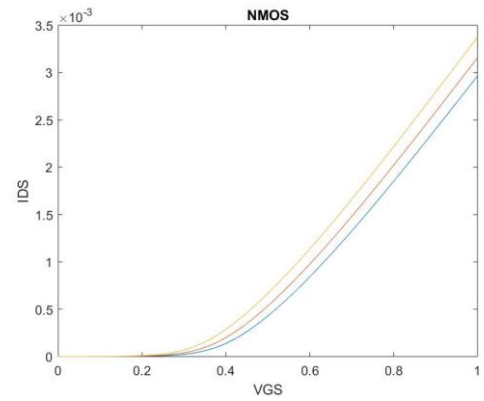
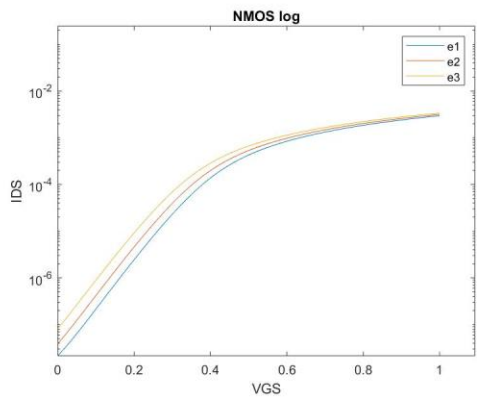
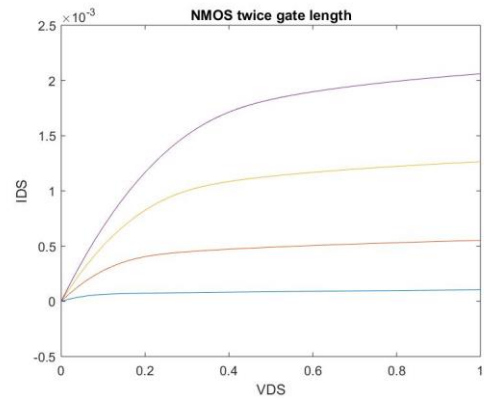


ECE1388 VLSI Design Methodology

Project-1 Report

Basamsetty Sai Anirudh(1006042747)

## Q.1

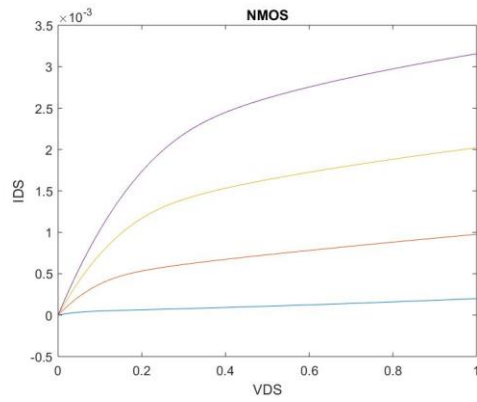

The graphs above show the VI characteristics of PMOS and NMOS in cadence 6. The graphs for different gate and source voltages were generated using parametric analysis.

**Procedure:**

The following connections were made for NMOS

- Gate: 1 V DC input from VDC
- Source: Grounded
- Drain: VDD of 1V dc from VDC
- Substrate: Grounded

The following connections were made for Pmos:

- Gate: -1 V DC input from VDC
- Source: VDD of -1V dc from VDC
- Drain: Grounded
- Substrate: VDD of -1V dc from VDC


Then the graphs were plotted using DC analysis in ADE L by fixing VGS and varying VDS and vice versa.

## Q 2.1

By studying the transient analysis and changing the capacitor value, the best capacitor value that reduces the values of delay from c to d and c to g is 11f F. Hence the value of gate capacitance of 64/32 is **11f F**. The delay was found to be 10.81f s

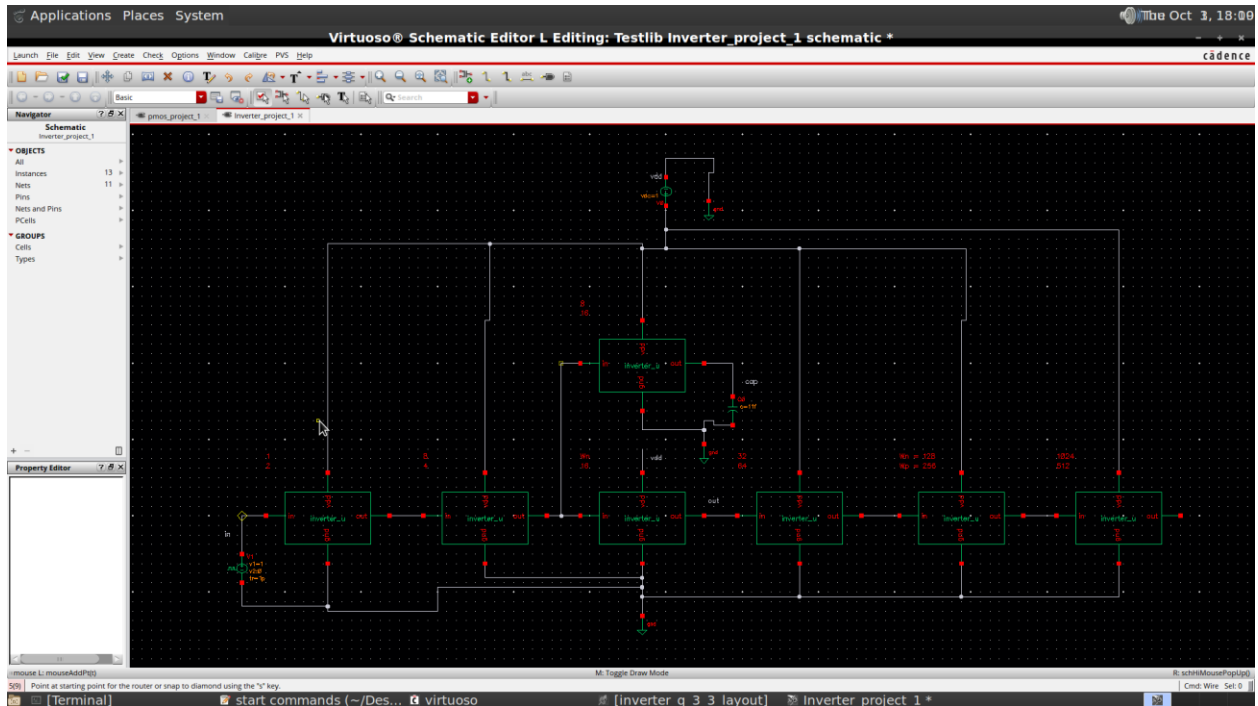**Procedure:**

The following circuit was designed by using the inverter cell and the values of Wp and Wn are specified as mentioned in the question i.e.(2/1,8/4,16/8,16/8,64/32,256/128,1024/512). The delay was calculated at the capacitor and at the input of the 4<sup>th</sup> inverter. By changing the value of capacitor the gate capacitance was determined.




The value of gate capacitance of 64/32 is 11f F . The delay was found to be 10.81f s

## Q 2.2

The value of  $R_p$  is 1.7 k $\Omega$

The value of  $R_n$  is 3.6 k $\Omega$

Procedure:

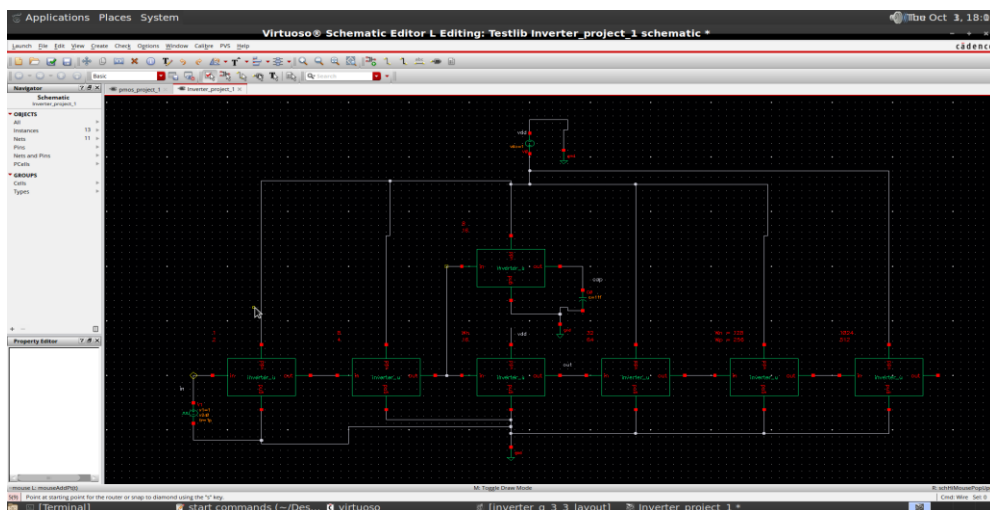

The following circuit was designed and the propagation delay was measured across 64/32 inverter having a fanout of 4(i.e 256/128). After the rising and falling delays were measured the circuit was modified such that 64/32 has a fanout of 5(i.e 320/160) and the delays were calculated.

To calculate the effective resistance


$$\Delta t_{pdr} = \frac{R_p}{2} (3 \times 4 \times C + 3C_d) - \frac{R_p}{2} (3 \times 3 \times C + 3C_d) = \frac{3}{2} R_p C$$

$$\Delta t_{pdf} = R_n (3 \times 4 \times C + 3C_d) - R_n (3 \times 3 \times C + 3C_d) = 3R_n C$$

We get  $\Delta t_{pdr}=1.87\text{ps}$ ,  $\Delta t_{pdf}=1.78\text{ps}$ ,  $C=11\text{fF}$ (from 2.1)

On substituting the values we get  $R_p=54\Omega \times 32=1.7\text{k}\Omega$  and  $R_n=113\Omega \times 32=3.6\text{k}\Omega$

## Q 2.3

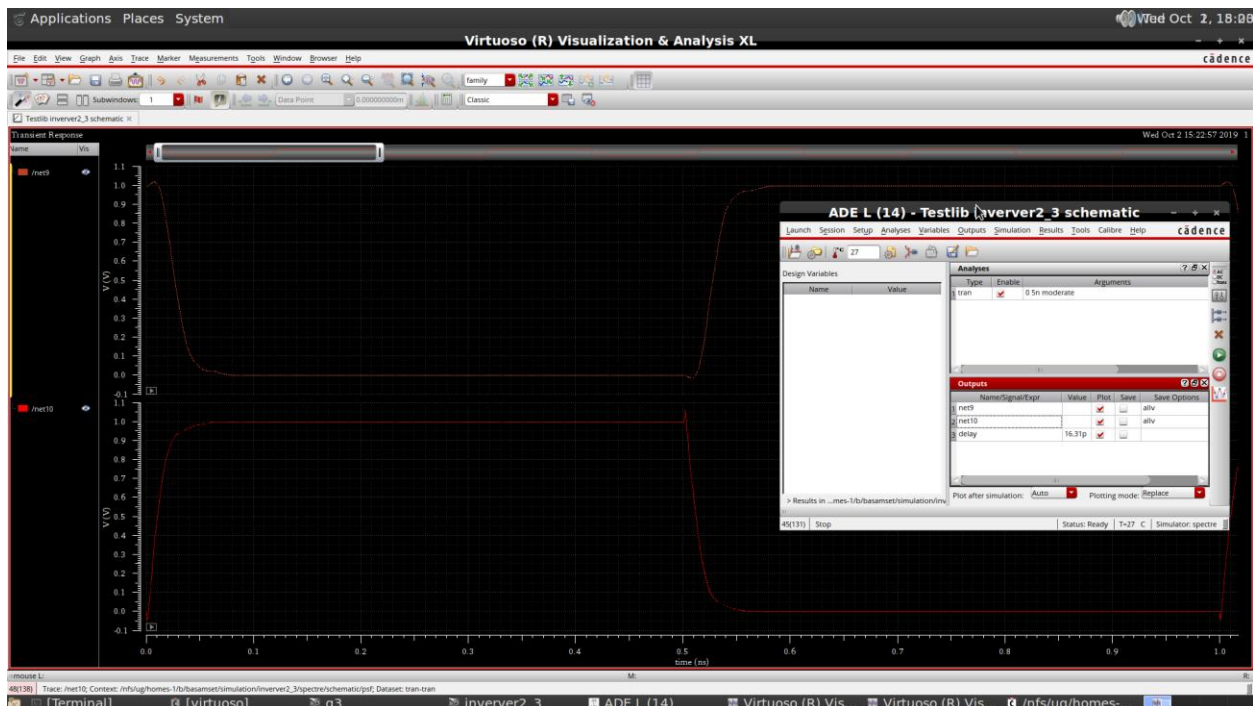

The input for the circuit is given as a step(rise time=1ps and fall time=1ps and period=1ns) and the delay was calculated as 16.31ps. The percentage difference between the delays is 1.9%



The circuit was modified according to the question and transient analysis was done to get the graphs and delay value.

Delay in Question 2.1 is 16.63Ps

**Calculation of percentage dealay:  $(16.63-16.61)/16.61 \times 100 = 1.926\%$**
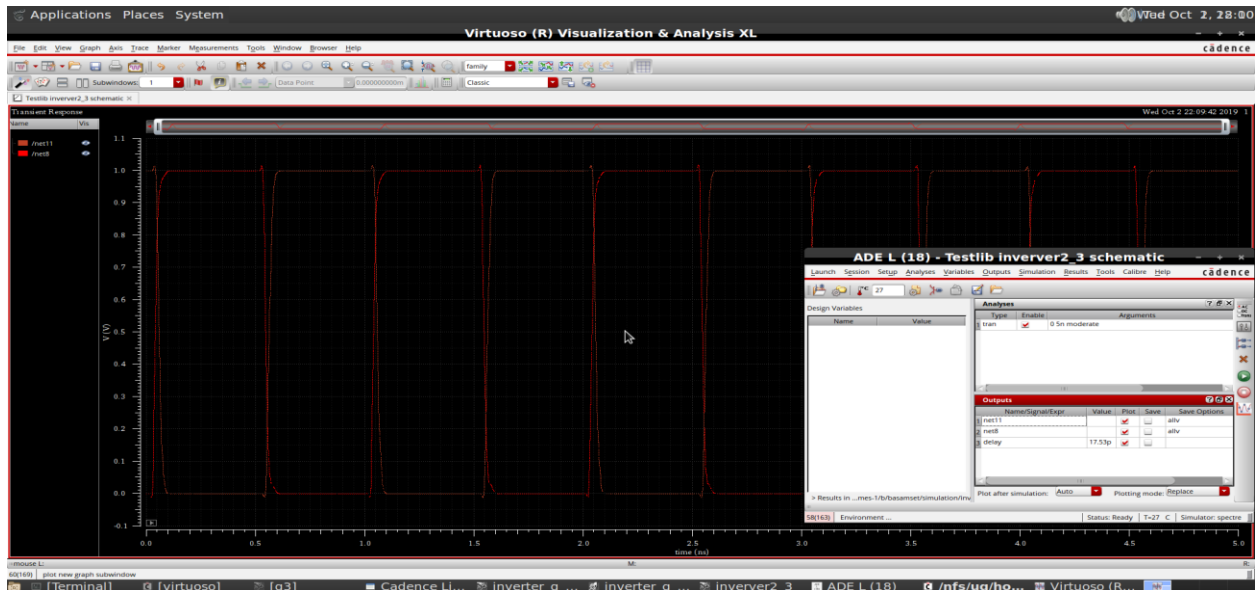 
## Q2.4


The circuit was modified as shown by changing the Wp and Wn values as in below figure



The delay for the 64/32 inverter was found to be 17.53ps and the percentage delay between the delay in question 2.1 and question 2.4 is **5.1%**.

**Calculation of percentage delay= (17.53-16.63)/17.53\*100=5.1%**

## Q 3.1

 

The transfer characteristics of an inverter are plotted by using parametric analysis (i.e.  $V_{GS}=0$  to  $1V$  and  $V_{DD}=1V$ ). The slope for the curve was found using the derivative function in the cadence calculator. The corresponding Y-axis values were found. ( $V_{IL}=420mV$ ,  $V_{OL}=53.3275mV$ ,  $V_{IH}=600mV$ ,  $V_{OH}=926.697mV$ )

The noise margins were calculated using the following formulas

$$N_{ML} = V_{IL} - V_{OH} \quad (420mV - 53.3275mV)$$

$$N_{MH} = V_{OH} - V_{IH} \quad (926.697mV - 600mV)$$

On substituting the values we get

$$\text{High Noise Margin (NMH)} = 366.6795mV$$

$$\text{Low Noise Margin (LMH)} = 326.697mV$$

## Q 3.2

After a trial and error analysis of making the high noise margin and low noise margin equal, the best value for  $W_p$  was found to be 45 where the noise margins were found to be 348.342 and 346.92

### Iteration 1:

$$W_p = 50$$

$$V_{IL} = 420mV, V_{OL} = 58.393mV, V_{IH} = 580mV, V_{OH} = 901.935mV$$

$$\text{High Noise Margin (NMH)} = 375.0223mV$$

$$\text{Low Noise Margin (LMH)} = 312.535mV$$


**Iteration 2:**

**Wp=64**

VIL=400mV, VOL= 51.4365 mV, VIH= 948.57 mV ,VOH= 600mV

**High Noise Margin(NMH)=348.46mV**

**Low Noise Margin(LMH)= 338.57mV**

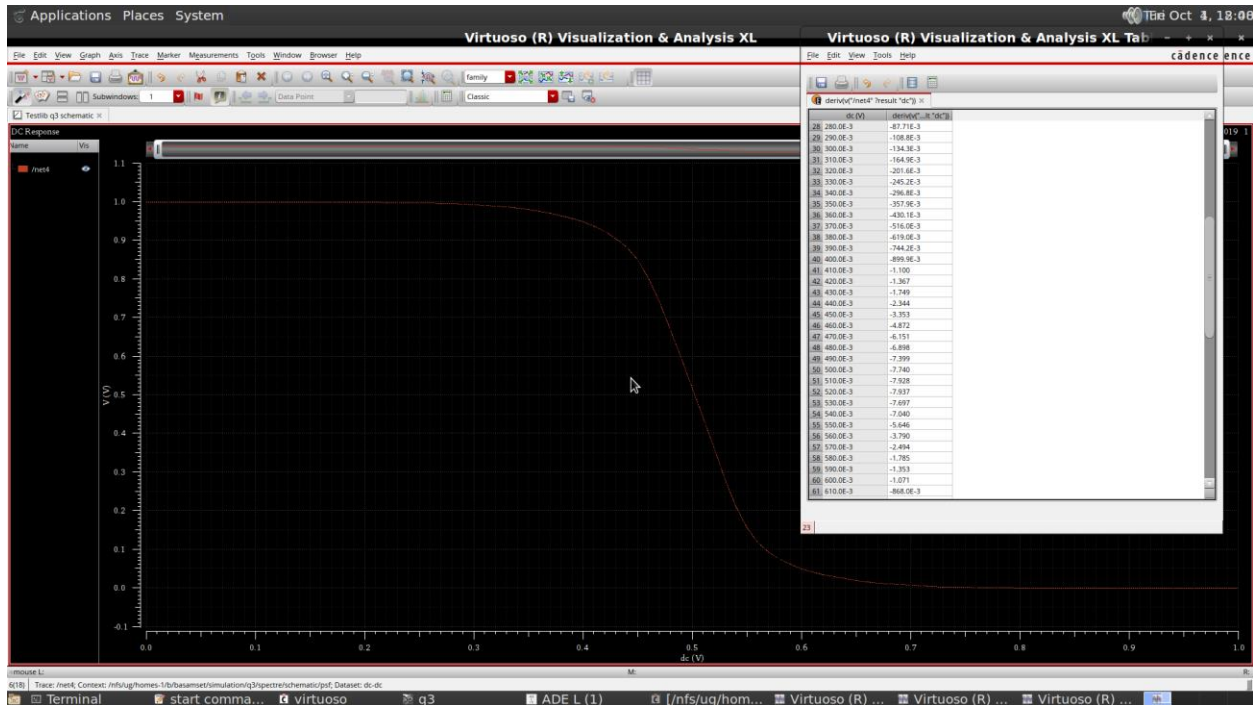


**For Wp=64 the values of high noise margin and low noise margins are almost equal.**

**Q 3.3**

 **From Q 3.2 the wp is found to be 64 and wn=32. So in the layout**





LVS report

```
#####
##                                ##
##  CALIBRE SYSTEM              ##
##                                ##
##  LVS REPORT                  ##
##                                ##
#####
```

**REPORT FILE NAME:** inverter\_q\_3\_3.lvs.report

**LAYOUT NAME:** /nfs/ug/homes-1/b/basamset/IC6CRN65GP/./CalibreLVS/inverter\_q\_3\_3.sp ('inverter\_q\_3\_3')

**SOURCE NAME:** /nfs/ug/homes-1/b/basamset/IC6CRN65GP/./CalibreLVS/inverter\_q\_3\_3.src.net ('inverter\_q\_3\_3')

**RULE FILE:** /nfs/ug/homes-1/b/basamset/IC6CRN65GP/./CalibreLVS/\_calibre.lvs\_

**CREATION TIME:** Fri Oct 4 17:27:20 2019

**CURRENT DIRECTORY:** /nfs/ug/homes-1/b/basamset/IC6CRN65GP/CalibreLVS

**USER NAME:** basamset

**CALIBRE VERSION:** v2014.3\_35.26 Wed Oct 1 13:01:36 PDT 2014

## OVERALL COMPARISON RESULTS

CELL COMPARISON RESULTS ( TOP LEVEL )

```
# ##### --
# # # * *
# # # CORRECT # |
```

```

# #      #      #      \  /
#      #####

```

LAYOUT CELL NAME: inverter\_q\_3\_3  
 SOURCE CELL NAME: inverter\_q\_3\_3

#### INITIAL NUMBERS OF OBJECTS

	Layout	Source	Component Type
	-----	-----	-----
Ports:	4	4	
Nets:	4	4	
Instances:	4	1	* MN (4 pins)
	4	1	* MP (4 pins)
	-----	-----	
Total Inst:	8	2	

#### NUMBERS OF OBJECTS AFTER TRANSFORMATION

	Layout	Source	Component Type
	-----	-----	-----
Ports:	4	4	
Nets:	4	4	
Instances:	1	1	_invv (4 pins)
	-----	-----	
Total Inst:	1	1	


\* = Number of objects in a layout different from the number in source.

\*\*\*\*\*  
 \*\*\*\*\*

#### INFORMATION AND WARNINGS

\*\*\*\*\*  
 \*\*\*\*\*

	Matched Layout	Unmatched Source	Unmatched Layout	Unmatched Source	Component Type
Ports:	4	4	0	0	
Nets:	4	4	0	0	
Instances:	1	1	0	0	_invv
<b>Total Inst:     1     1     0     0</b>					

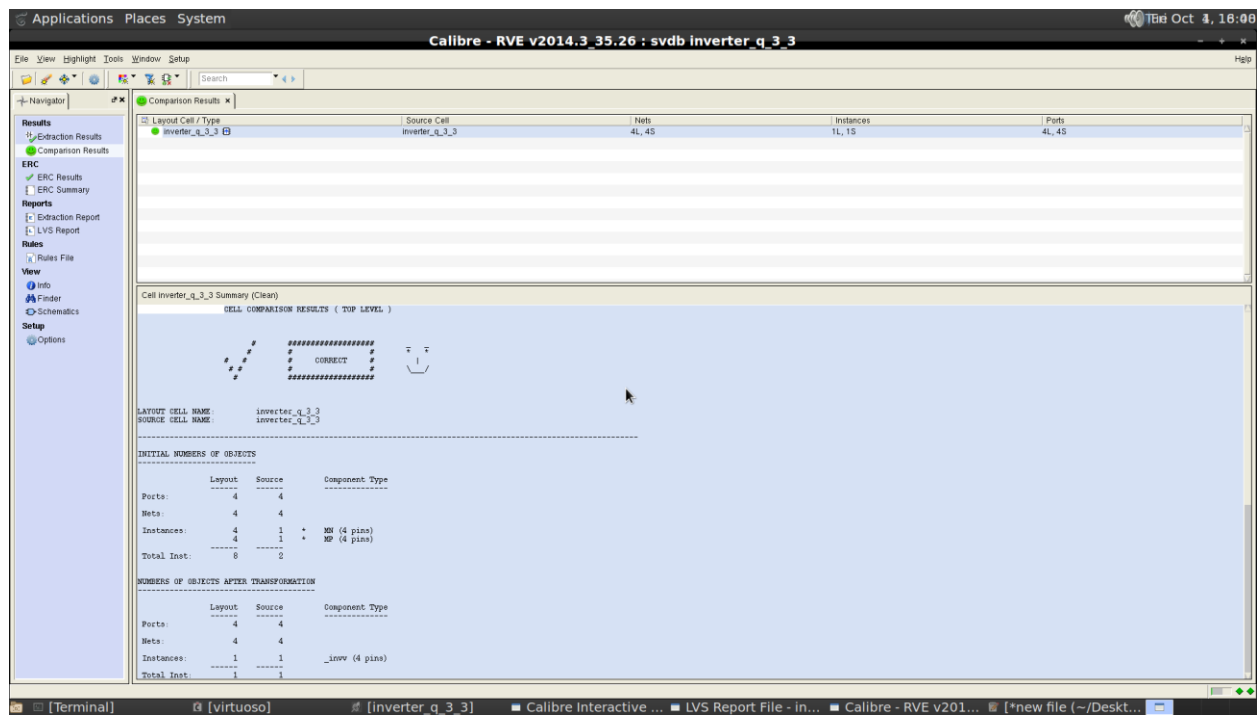

#####  
 ##  
 ## CALIBRE SYSTEM ##  
 ##

## ## CIRCUIT EXTRACTION REPORT ##

##

##

#####

**REPORT FILE NAME:** inverter\_q\_3\_3.lvs.report.ext

**LAYOUT NAME:** inverter\_q\_3\_3.calibre.db ('inverter\_q\_3\_3')


**CREATION TIME:** Fri Oct 4 16:47:25 2019

**CURRENT DIRECTORY:** /nfs/ug/homes-1/b/basamset/IC6CRN65GP/CalibreLVS

**USER NAME:** basamset

**CALIBRE VERSION:** v2014.3\_35.26 Wed Oct 1 13:01:36 PDT 2014

### Extracted layout

 

The values of extracted layout were found as  $V_{il}=390\text{mV}$ ,  $V_{ol}=55.1099$ ,  $V_{ih}=570\text{mV}$ ,  $V_{oh}=936.669$ ,  $580\text{mV}$

**Low Noise Margin (LMH)  $300.38\text{mV}$**

**High Noise Margin (NMH)  $=366.66\text{mV}$**

And the values from question 3.1 are

**High Noise Margin(NMH)  $=366.6795\text{mV}$**

**Low Noise Margin(LMH)=326.697mV which are nearly equal.**